

Week 11: Chap. 16a Pulse Processing


Fast Neutron Detection

Pulse Processing (passive)

- Signal shape
- Cable properties
- connectors
- impedance
- CR, RC filters

Pulse Processing (active)

Big RIPS Electronics
RIKEN, April, 2017

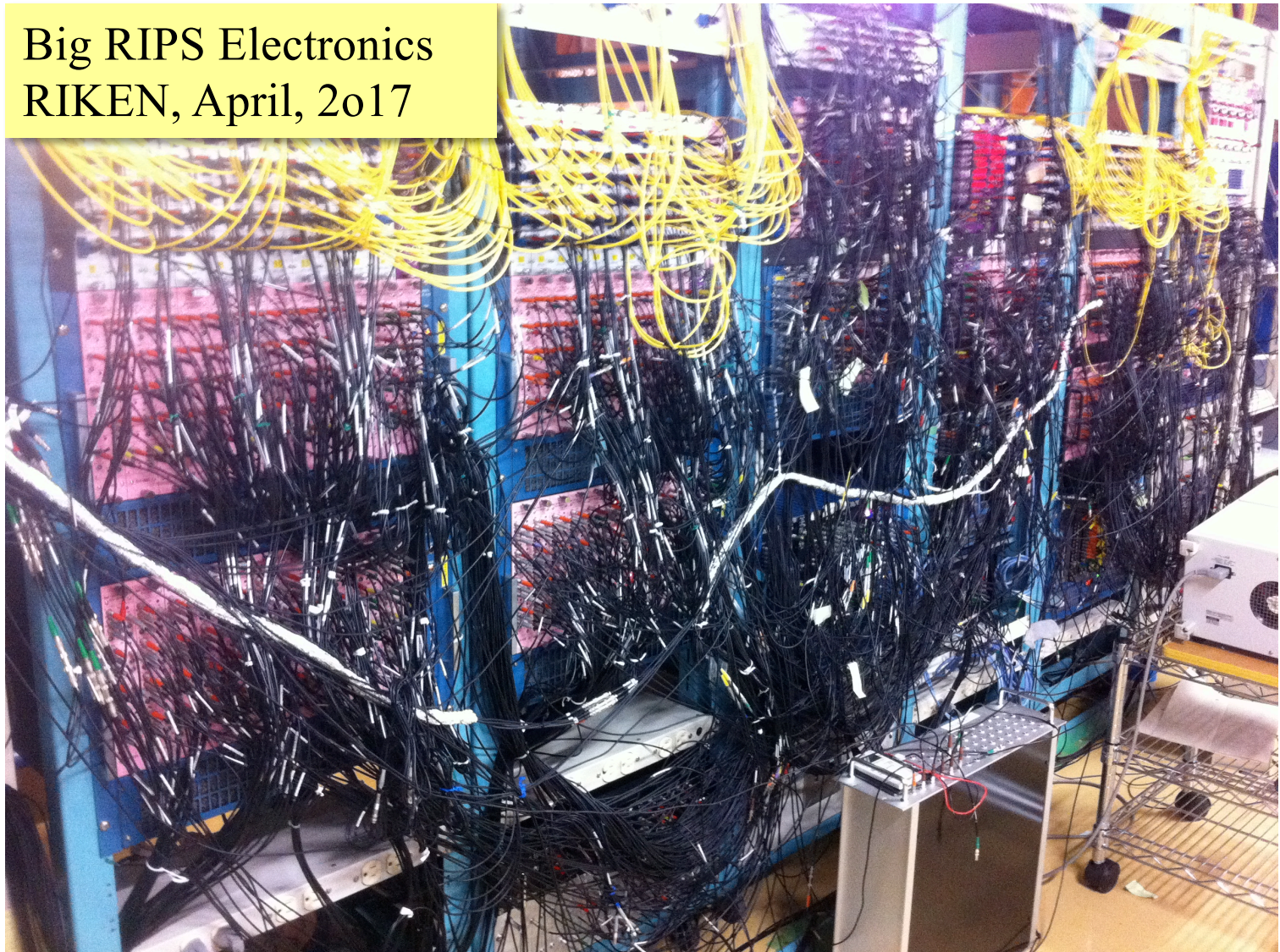

Pulse Processing: overview

Fig. 16.1 Knoll, 4th Ed.



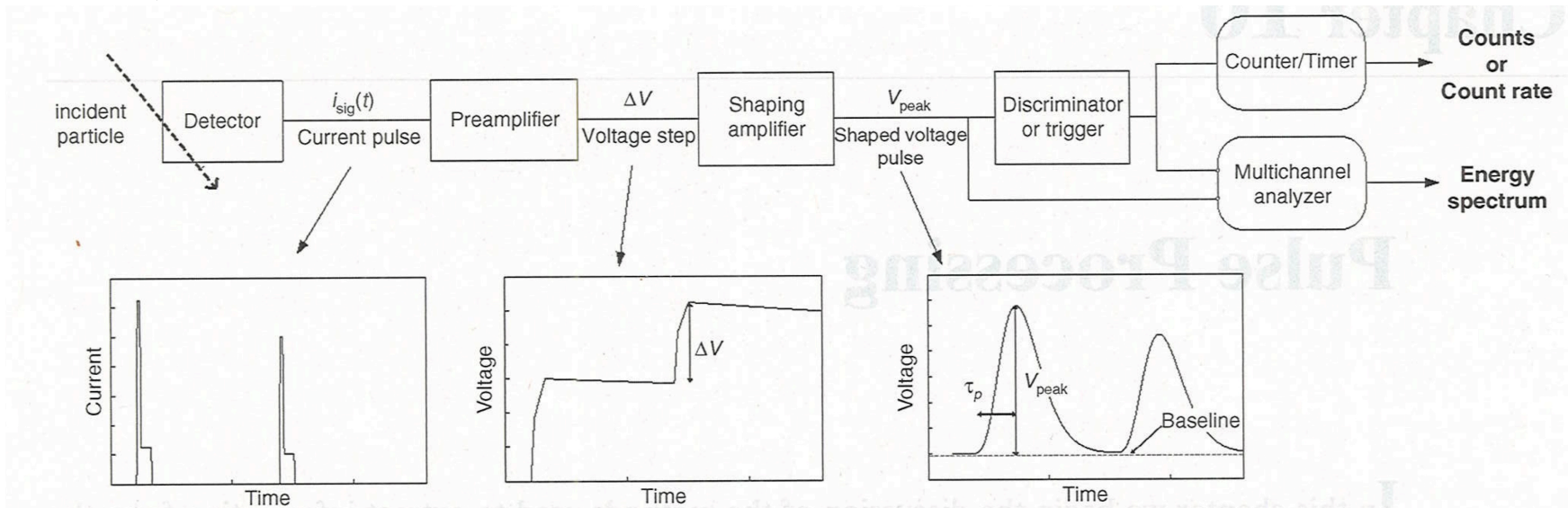
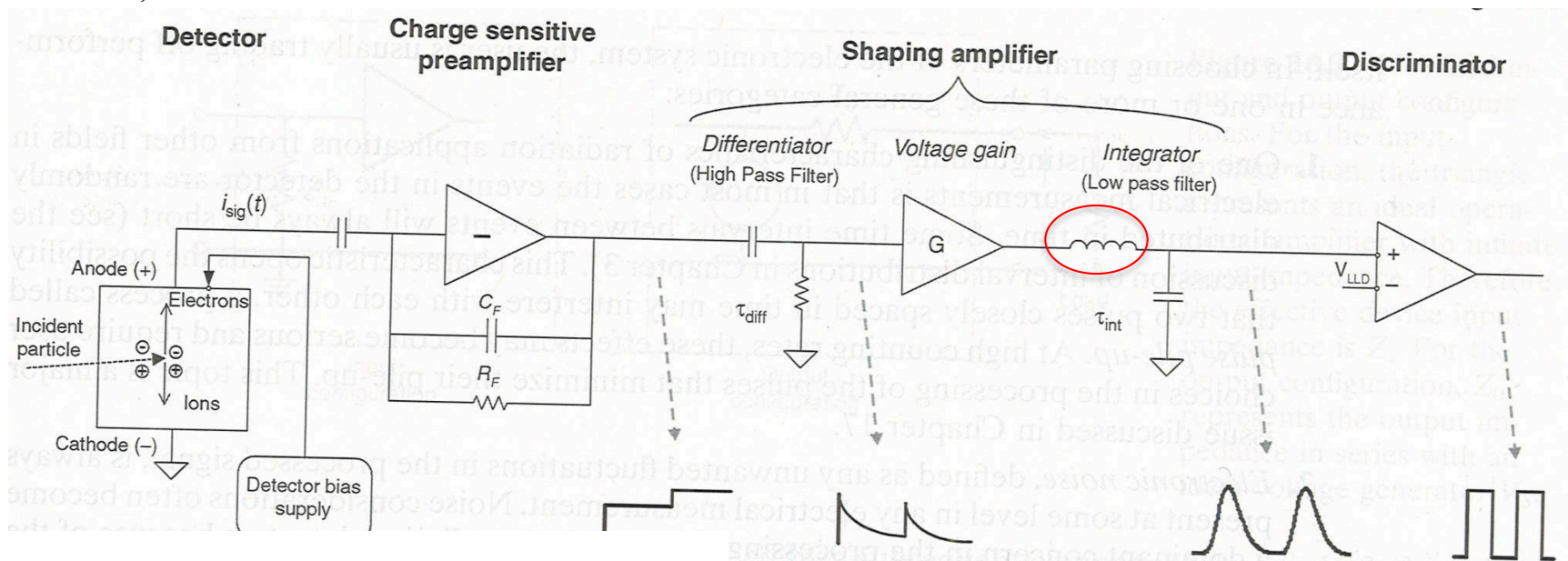


Fig. 16.2 Knoll, 4th Ed.

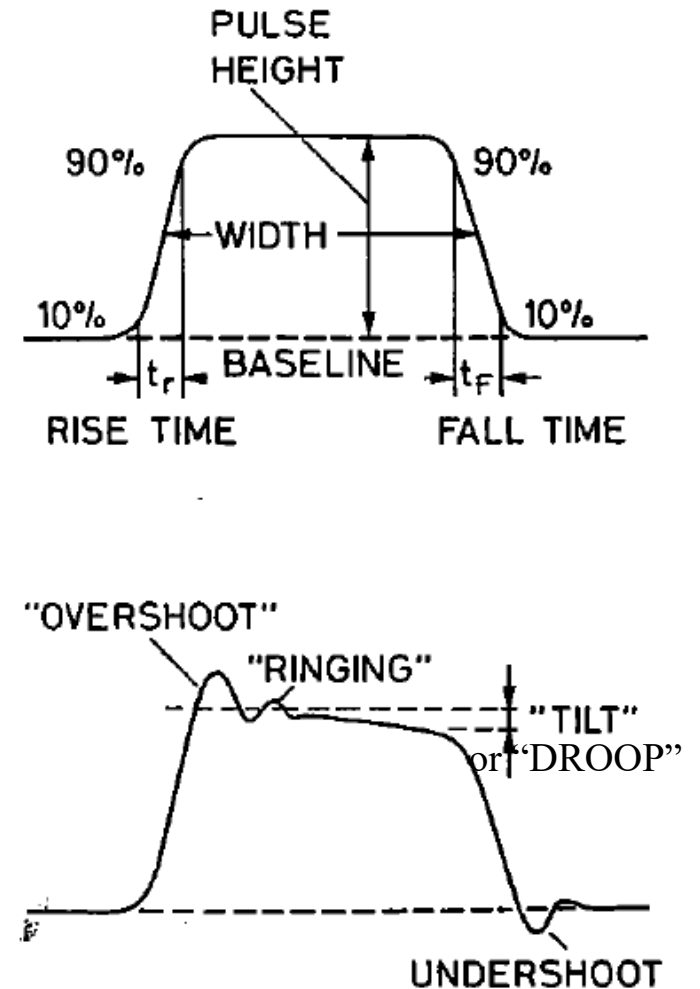

Chap. 16a – Pulse Processing

Fig. 4.1 Knoll, 3rd, 4th Eds.

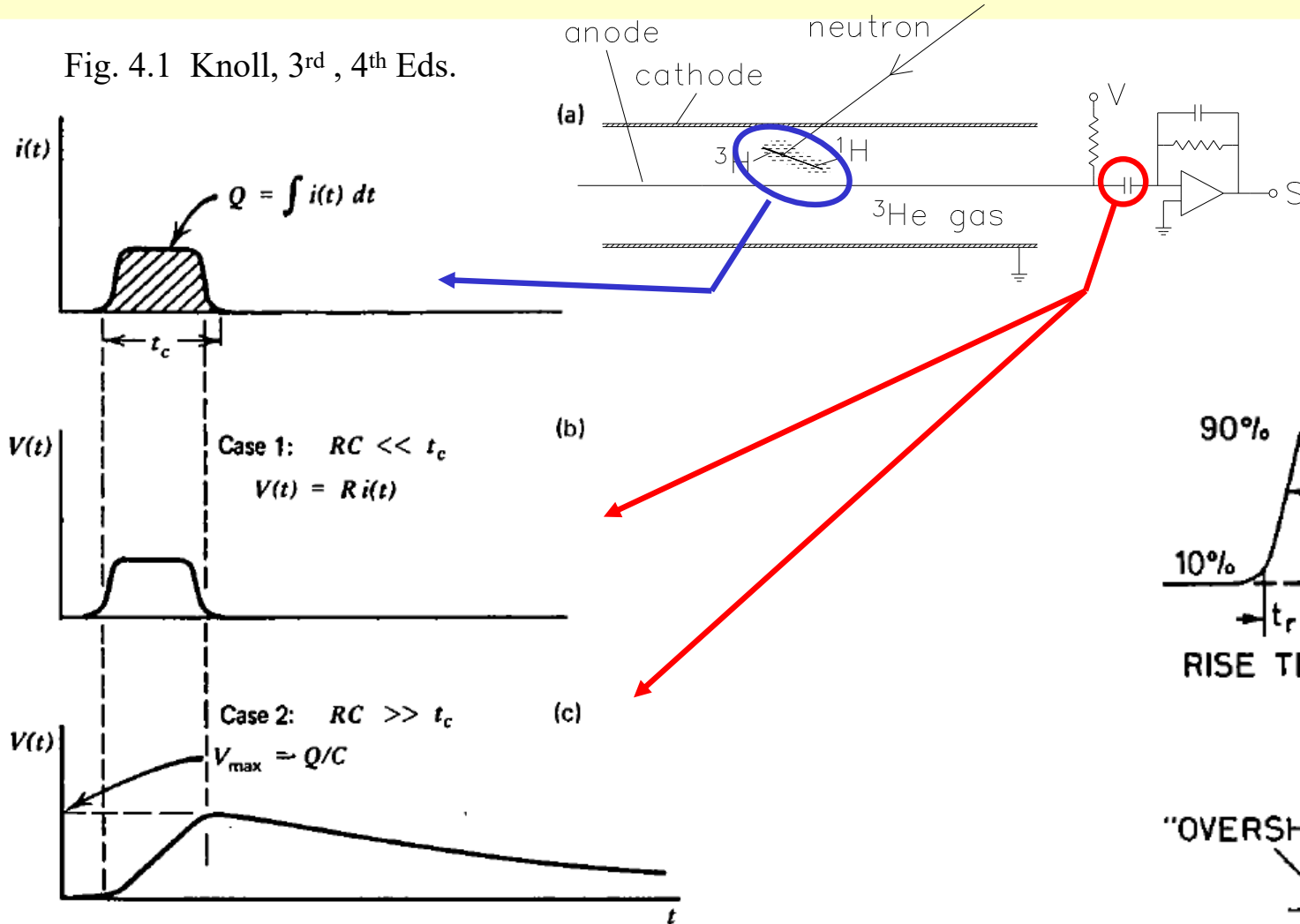


Leading or Falling edge
 Rise or Fall time – 10:90%
 (Uni or Bipolar // Analog or Digital)


Fig. 11.1 Leo, 2nd Ed.

Pulse Processing: cables

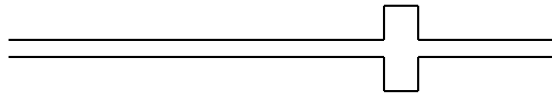Twisted pairs – “differential” signals, analogue or logic




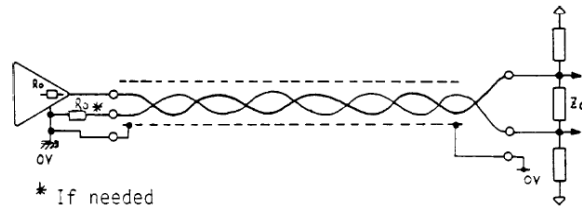Shielded Twisted Pair Cable True Differential Input





* If needed

Coaxial Cable - Single-Ended Connection

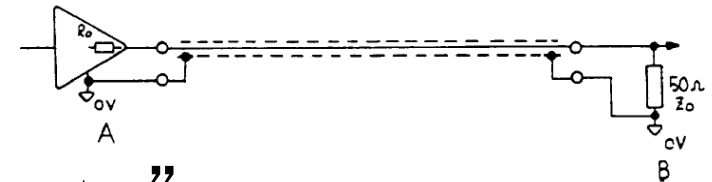

Coaxial conductor/shield – signal on the “center”

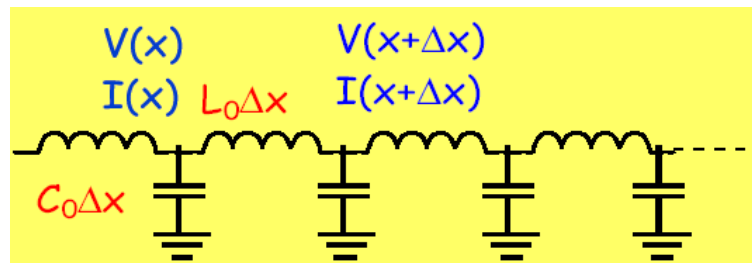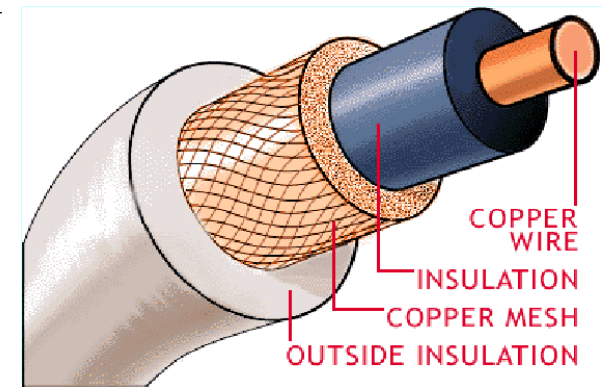Each configuration has a RG/U name with a characteristic capacitance and inductance per unit length, and an impedance (with a negligible resistance).



$$\frac{d^2V}{dx^2} = -\omega^2 L_0 C_0 V$$

$$V = Ae^{jkx} + Be^{-jkx} \quad k^2 = \omega^2 L_0 C_0$$

$$v = \frac{\omega}{k} = \frac{1}{\sqrt{L_0 C_0}}$$


$$Z_0 = \sqrt{\frac{L_0}{C_0}}$$

for coax

$$C_0 = 2\pi\epsilon / \ln(r_2 / r_1)$$

$$L_0 = (\mu / 2\pi) \ln(r_2 / r_1)$$


Pulse Processing: some connectors

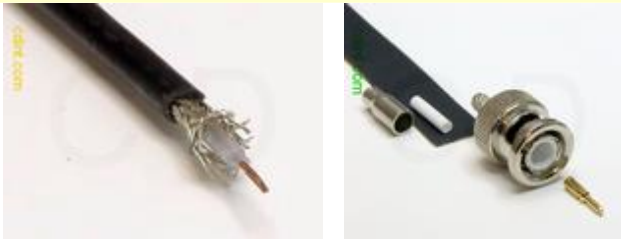


<http://www.cdint.com/catalog/model/CC-B>

<https://www.amphenolrf.com/connectors/bnc.html>

“BNC is an acronym for Bayonet Neill-Concelman, after Paul Neill of Bell Labs (inventor of the N connector) and Amphenol engineer Carl Concelman (inventor of the C connector). BNC is often erroneously expanded to "Baby Neill-Concelman", "Baby N connector", "British Naval Connector", "Bayonet Nut Connector”, “Bayonet Network Connector”, “Barrel Nut Connector”, “Bayonet N-type Compact”, “Berkeley Nucleonics Corp.” ...

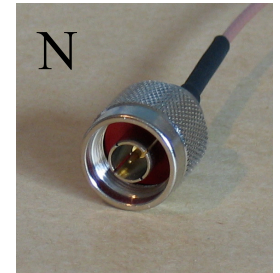


“This connector has a characteristic impedance of 50 ohms, and needs to be mated with 50 ohm coaxial cable in order to prevent signal loss, noise, and/or transmitter damage due to signal reflections at the point of mismatch. 50 ohm coax cable, connectors, and adapters are commonly used in co-ax wifi cables (old school, 802.11 wireless LAN) antennas, ham transceivers, and other radio frequency (RF) analog and digital signaling, microwave, radar, hi-fidelity professional audio, non-destructive testing (NDT), oil and petroleum production, ultrasonic transducers, accelerometers, strain gauges, and some professional video applications.”

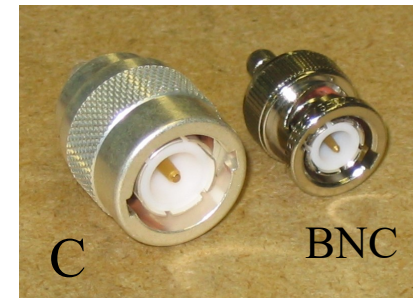

LEMO documentation

<http://www.lemo.com/en/documentation>

(Léon Mouttet)

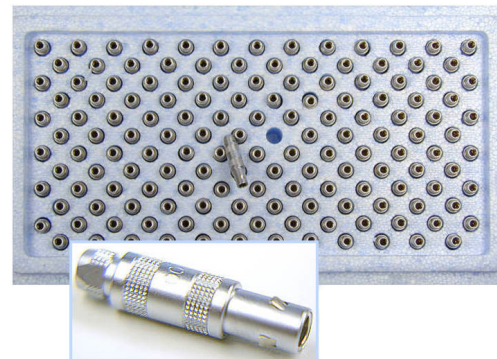


LEMO to BNC

Pulse Processing: impedance matching

Fig. 16.4 Knoll, 3rd Ed.

16.7, 4th Ed.

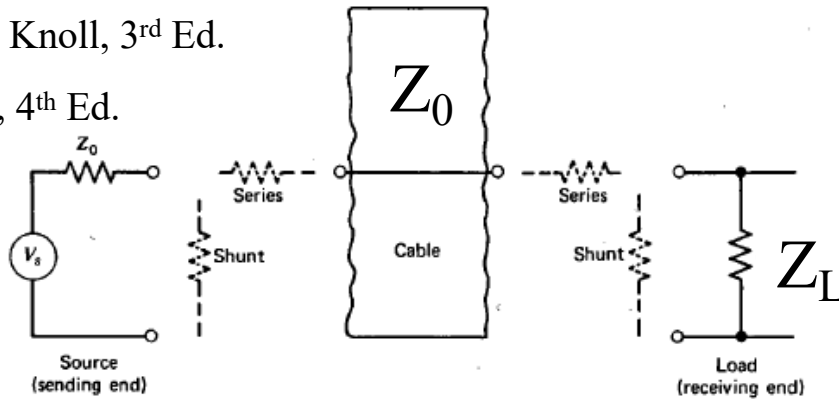

What happens if: ?

$$I_{\text{Inc}} + I_{\text{refl}} = I_L$$

$$V_{\text{Inc}} + V_{\text{refl}} = V_L$$

$$V_{\text{refl}} = -I_{\text{refl}} Z_0$$

$$\rightarrow \frac{V_{\text{refl}}}{V_{\text{Inc}}} = \frac{Z_L - Z_0}{Z_L + Z_0}$$


$$\frac{V_L}{V_{\text{Inc}}} = \frac{2Z_L}{Z_L + Z_0}$$

- Open circuit .. $Z_L \sim \infty$
- Short circuit .. $Z_L = 0$
- Match circuit .. $Z_L = Z_0$


Match to get maximum transmission to load (S/N), minimize reflections (ringing), maintain signal shape.

Don't Match to minimize transmission .. Weak signals into high impedance loads or low power sources (but must use short cables).

Pulse Processing: simplest manipulations

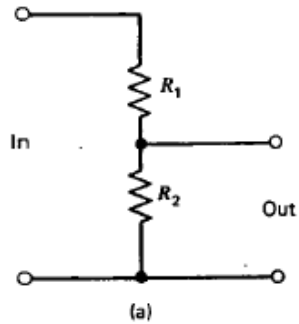

Voltage divider (recall PMT base)

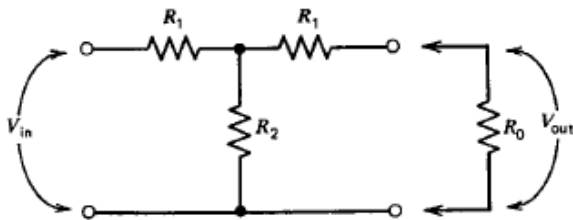

$$\text{Attenuation } \alpha = V_{\text{out}}/V_{\text{in}}$$

$$R_1 = R_0 \frac{\alpha - 1}{\alpha + 1}$$

$$R_2 = R_0 \frac{2\alpha}{\alpha^2 - 1}$$

Fig. 16.5 Knoll, 3rd Ed.

16.8, 4th Ed.

Signal splitter: $R = R_0/3$

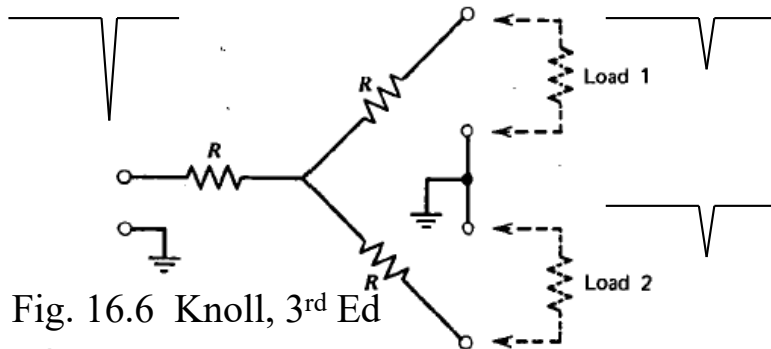


Fig. 16.6 Knoll, 3rd Ed

16.9, 4th Ed..

Signal Inverter

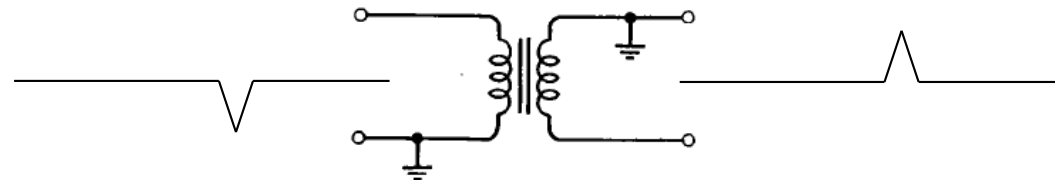


Fig. 16.7 Knoll, 3rd Ed.




16.10 4th Ed.

All loads must be present, or else see previous discussion about reflections!

Pulse Processing: CR circuit

Fig. 16.9 Knoll, 3rd Ed.

17.2 4th Ed.

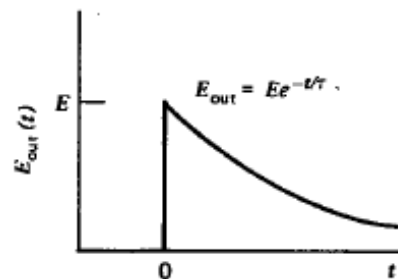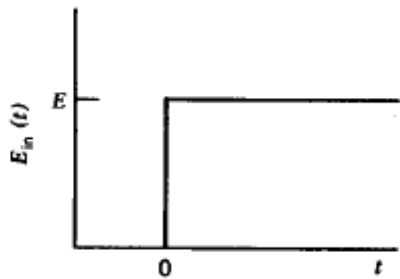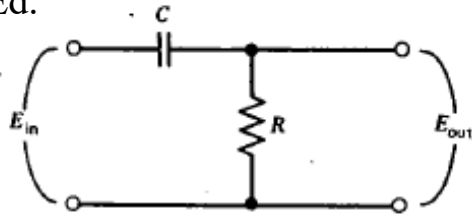

$$V_{in} = \frac{Q}{C} + V_{out} \quad (C \text{ is constant})$$

$$\frac{dV_{in}}{dt} = \frac{1}{C} \frac{dQ}{dt} + \frac{dV_{out}}{dt} \quad \frac{dQ}{dt} = i = V/R$$

$$\frac{dV_{in}}{dt} = \frac{V_{out}}{RC} + \frac{dV_{out}}{dt} \quad \tau = RC$$

$$\tau \frac{dV_{in}}{dt} = V_{out} + \tau \frac{dV_{out}}{dt}$$

$$V_{out} \approx \tau \frac{dV_{in}}{dt} \quad \text{for small } \tau$$

$$\tau \frac{dV_{out}}{dt} \approx \tau \frac{dV_{in}}{dt} \quad \text{for large } \tau$$



$$V_{out} \approx V_{in}$$

The differentiator (when τ is small, “fast” electronics)
 .. Should remove low frequency components and is called a
 “high-pass” filter.

Pulse Processing: RC circuit

Fig. 16.9 Knoll, 3rd Ed.

17.3, 4th Ed.

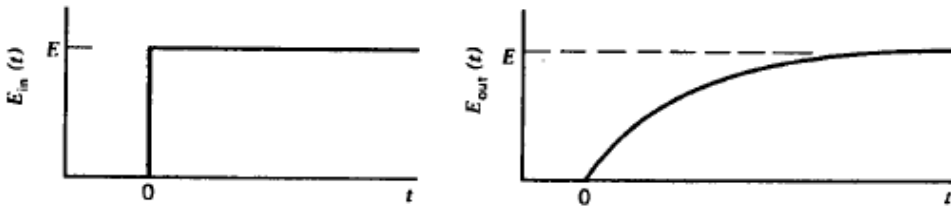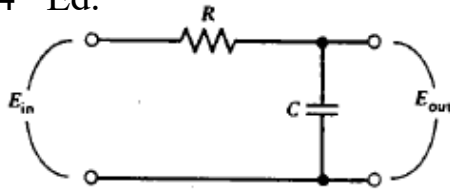

$$V_{in} = iR + V_{out}$$

$$i = \frac{dQ}{dt} = C \frac{dV_{out}}{dt} \quad (\text{on capacitor})$$

$$V_{in} = RC \frac{dV_{out}}{dt} + V_{out}$$

$$V_{in} = \tau \frac{dV_{out}}{dt} + V_{out}$$

$$\frac{V_{in}}{\tau} \approx \frac{dV_{out}}{dt} \rightarrow \frac{1}{\tau} \int V_{in} dt \approx V_{out}$$

$$V_{out} \approx V_{in} \quad \text{for small RC}$$

The integrator (when τ is large, “slow” electronics)
 .. Should remove high frequency components and is called a
 “low-pass” filter.

Pulse Processing: Cable Properties

$$v = \frac{\omega}{k} = \frac{1}{\sqrt{L_0 C_0}}$$

$$Z_0 = \sqrt{\frac{L_0}{C_0}} \rightarrow Z_0^2 C_0 = L_0$$

$$v = \frac{\omega}{k} = \frac{1}{\sqrt{Z_0^2 C_0^2}} = \frac{1}{Z_0 C_0}$$

A velocity has dimensions of (length / time)
 The time depends on the length of the real cable.
 Some example properties from Belden Cables:

	58 /U	59 /U	213/U	316 /U
Z ₀	50 Ω	75	50	50
C ₀	24.3 pF/ft	16.3	30.8	29
L ₀	0.064 μH/ft	0.107	0.077	0.067
v/c	0.77	0.83	0.66	0.695
τ	1.2 ns/ft (4 ns/m)	1.3 ns/ft	1.5 ns/ft	1.4 ns/ft

Pulse Processing: Cable Consequences

$$v = \frac{\omega}{k} = \frac{1}{\sqrt{L_0 C_0}}$$

$$Z_0 = \sqrt{\frac{L_0}{C_0}} \rightarrow Z_0^2 C_0 = L_0$$

$$v = \frac{\omega}{k} = \frac{1}{\sqrt{Z_0^2 C_0^2}} = \frac{1}{Z_0 C_0}$$

A velocity has dimensions of (length / time)
 The time depends on the length of the real cable.
 Some example properties from Belden Cables:



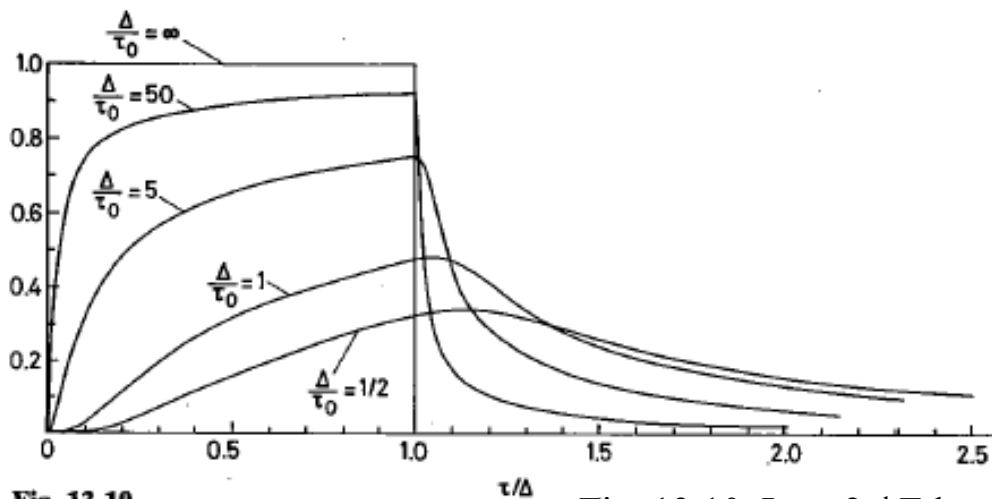


Fig. 13.10

Fig. 13.10 Leo, 2nd Ed.

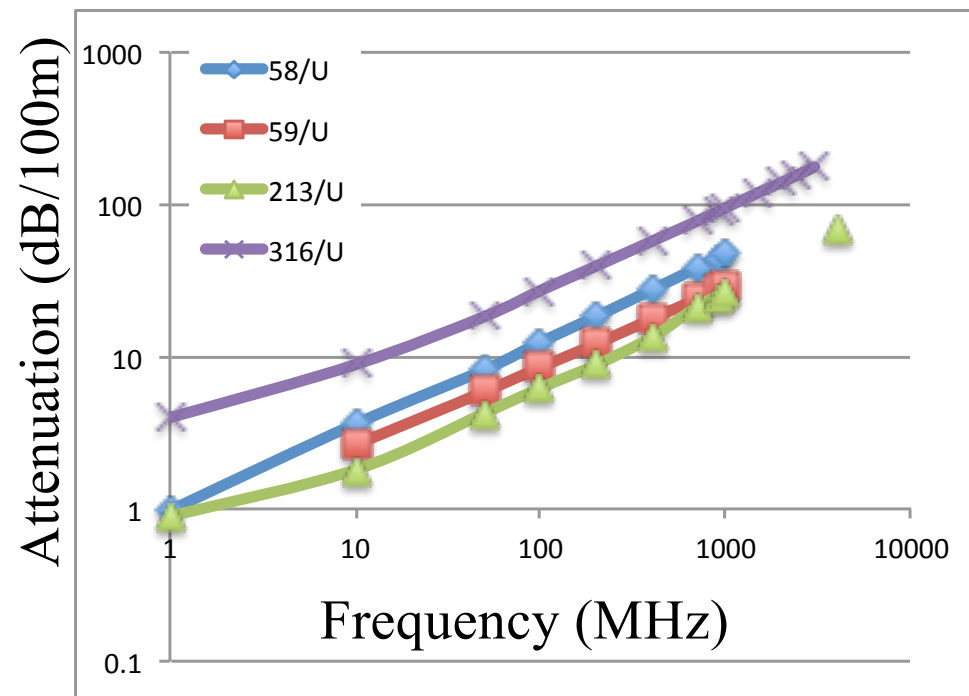

Pulse Processing: Question

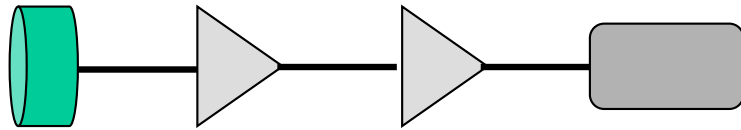


Electronics in the vault or not?



Compare the output of a preamp step-function pulse that passes through a 1m Beldin RG-58/U cable to that from passing through 50 m of the same cable. Use the Fermi function with $a=1$, $t_0=10$, $\tau = 4$ ns/m, and t in ns.

$$f(t) = 1/(1 + e^{-(t-t_0)/a})$$

Pulse Processing: Answer

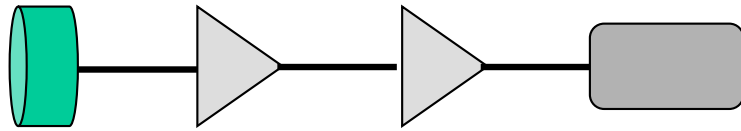

Electronics in the vault or not?



Compare the output of a preamp step-function pulse that passes through a 1m Beldin RG-58/U cable to that from passing through 50 m of the same cable. Use the Fermi function with $a=1$, $t_0=10$, $\tau = 4$ ns/m, and t in ns.

